

1. The maximum clock frequency in MHz of a 4-stage ripple counter, utilize flip-flops, with each flip-flop having a propagation delay of 20 ns, is _____.
(round off to one decimal place)